

Direct Current Electricity **14-7a**

DC Circuits

Resistivity

$$R = \frac{\rho L}{A} \quad 44.1$$

Depends on temperature:

$$\rho = \rho_0 (1 + \alpha (T - T_0)) \quad 44.2$$

$$R = R_0 (1 + \alpha (T - T_0)) \quad 44.3$$

Example (FEIM):
A cube with an edge length of 0.01 m has resistivity of 0.01 $\Omega \cdot \text{m}$.
What is the resistance from one side to the opposite side?

(A) 0.0001
(B) 0.001
(C) 0.1
(D) 1

$$R = \frac{\rho L}{A} = \frac{(0.01 \Omega \cdot \text{m})(0.01 \text{ m})}{(0.01 \text{ m})^2} = 1 \Omega$$

Therefore, the answer is (D).

Professional Publications, Inc. FERC

Direct Current Electricity

14-7b

DC Circuits

Ohm's Law

$$V = IR \quad 44.22$$

Resistors in Series:

$$R_S = R_1 + R_2 + \cdots + R_n \quad 44.4$$

Resistors in Parallel:

$$R_P = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \cdots + \frac{1}{R_n}} \quad 44.5$$

Equivalent resistance of two resistors in parallel:

$$R_P = \frac{R_1 R_2}{R_1 + R_2} \quad 44.6$$

Resistive Power

$$P = VI = \frac{V^2}{R} = I^2 R \quad 44.7$$

Professional Publications, Inc.

FERC


Direct Current Electricity

14-7c

DC Circuits

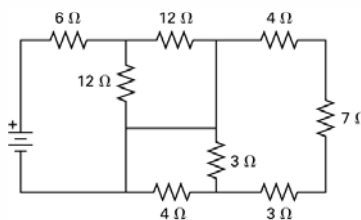Example (FEIM):

What is the resistance of the following circuit as seen from the battery?



No current will flow through the two $4\ \Omega$ resistors, the two $3\ \Omega$ resistors, or the $7\ \Omega$ resistor. The circuit reduces to one $6\ \Omega$ in series with two $12\ \Omega$ in parallel.

$$R = 6\ \Omega + 6\ \Omega = 12\ \Omega$$

Professional Publications, Inc.

FERC

Direct Current Electricity**14-7d****DC Circuits**

Kirchhoff's Laws

- Voltage Law (KVL)

$$\sum V_{\text{rises}} = \sum V_{\text{drops}} \quad [\text{closed path}] \quad 44.24$$

- Current Law (KCL)

$$\sum I_{\text{in}} = \sum I_{\text{out}} \quad [\text{closed surface}] \quad 44.23$$

Professional Publications, Inc.

FERC

Direct Current Electricity**14-7e****DC Circuits**

Loop Current Circuit Analysis

1. Select one less than the total number of loops.
2. Write Kirchhoff's voltage equation for each loop.
3. Use the simultaneous equations to solve for the current you want.

Professional Publications, Inc.


FERC

Direct Current Electricity

14-7f

DC Circuits

Example (FEIM):

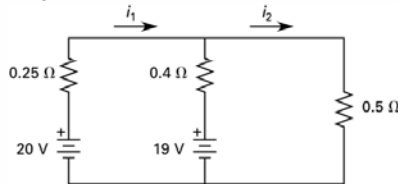Find the current through the $0.5\ \Omega$ resistor.

The voltage sources around the left loop are equal to the voltage drops across the resistances.

$$20\text{ V} - 19\text{ V} = 0.25\ \Omega\ i_1 + 0.4\ \Omega\ (i_1 - i_2)$$

The same is true for the right loop.

$$19\text{ V} = 0.4\ \Omega\ (i_2 - i_1) + 0.5\ \Omega\ i_2$$

Solve—two equations and two unknowns.

$$0.65\ \Omega\ i_1 - 0.4\ \Omega\ i_2 = 1\text{ V}$$

$$-0.4\ \Omega\ i_1 + 0.9\ \Omega\ i_2 = 19\text{ V}$$

$$i_1 = 20\text{ A}$$

$$i_2 = 30\text{ A}$$

The current through the $0.5\ \Omega$ resistor is 30 A.

Professional Publications, Inc.

FERC

Direct Current Electricity

14-7g

DC Circuits

Node Voltage Circuit Analysis

1. Convert all current sources to voltage sources.
2. Choose one node as reference (usually ground).
3. Identify unknown voltages at other nodes compared to reference.
4. Write Kirchhoff's current equation for all unknown nodes except reference node.
5. Write all currents in terms of voltage drops.
6. Write all voltage drops in terms of the node voltages.

Professional Publications, Inc.


FERC

Direct Current Electricity

14-7h

DC Circuits

Example (FEIM):

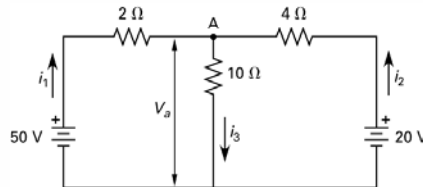Find the voltage potential at point A and the current i_1 .

$$i_1 + i_2 = i_3$$

$$\frac{50 \text{ V} - V_A}{2 \Omega} + \frac{20 \text{ V} - V_A}{4 \Omega} = \frac{V_A - 0}{10 \Omega}$$

$$V_A = 35.3 \text{ V}$$

$$i_1 = \frac{50 \text{ V} - V_A}{2 \Omega} = \frac{50 \text{ V} - 35.3 \text{ V}}{2 \Omega} = 7.35 \text{ A}$$

Professional Publications, Inc.

FERC

Direct Current Electricity

14-8a

Voltage Divider

The voltage across a resistor R in a loop with total resistance R_{total} with a voltage source V is

$$V_R = \frac{R}{R_{\text{total}}} V$$

In the general case, the voltage on impedance Z_i in a loop with total impedance Z_{total} with a voltage source v is

$$v_i = \frac{Z_i}{Z_{\text{total}}} v$$

NOTE: Each symbol is a complex number in the general case.

Professional Publications, Inc.


FERC

Direct Current Electricity

14-8b

Voltage Divider

Example (FEIM):

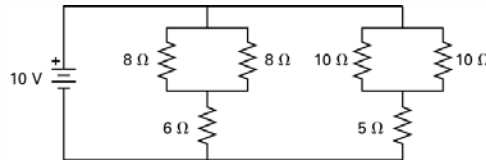What is the voltage across the 6 Ω resistor?

- (A) 5 V
(B) 6 V
(C) 8 V
(D) 10 V

Two 8 Ω resistors in parallel equal 4 Ω .The voltage across the 6 Ω resistor is

$$(10 \text{ V}) \left(\frac{6 \Omega}{6 \Omega + 4 \Omega} \right) = 6 \text{ V}$$

Therefore, the answer is (B).

Professional Publications, Inc.

FERC

Direct Current Electricity

14-9a

Current Divider

The current through a resistor R in parallel with another resistance R_{parallel} and a current into the node of I is:

$$I_R = \frac{R_{\text{parallel}}}{R_{\text{total}}} I \quad (\text{Resistance } R \text{ does not appear explicitly. } R_{\text{total}} \text{ is the sum of the resistances in parallel.})$$

In the general case, the current through impedance Z_i connected to a node in parallel with total impedance Z_{total} with a current i into the node is:

$$i_{Z_i} = \frac{Z_{\text{parallel}}}{Z_{\text{total}}} i \quad (Z_{\text{total}} \text{ is the sum of the impedances in parallel.})$$

NOTE: Each symbol is a complex number in the general case.

Procedure:

1. Identify the component you want the current through.
2. Simplify the circuit.
3. Determine the current into the node that is connected to the component of interest.
4. Allocate current in proportion to the reciprocal of resistance.

Professional Publications, Inc.

FERC

Direct Current Electricity

14-9b


Current Divider

Example (FEIM):

What is the current through the $6\ \Omega$ resistor?

- (A) $1/10\text{ A}$
- (B) $1/3\text{ A}$
- (C) $1/2\text{ A}$
- (D) 1 A

$$i = i_1 + i_2$$

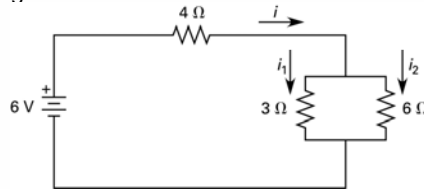

Simplify the circuit.

$$3\ \Omega \text{ in parallel with } 6\ \Omega = 2\ \Omega$$

$$2\ \Omega \text{ in series with } 4\ \Omega = 6\ \Omega$$

$$i = \frac{6\text{ V}}{6\ \Omega} = 1\text{ A}$$

$$R_{\text{parallel}} = 3\ \Omega$$

$$R_{\text{total}} = 3\ \Omega + 6\ \Omega = 9\ \Omega$$

$$i = (1\text{ A}) \left(\frac{3\ \Omega}{3\ \Omega + 6\ \Omega} \right) = 1/3\text{ A}$$

Therefore, the answer is (B).

Professional Publications, Inc.

FERC

Direct Current Electricity

14-10a

Superposition Theorem

The net current/voltage is the sum of the current/voltage caused by each current/voltage source.

Procedure:

1. Short all voltage sources, and open all current sources, then turn on only one source at a time.
2. Simplify the circuit to get the current/voltage of interest.
3. Repeat until all sources have been used.
4. Add the results for the answer.

Professional Publications, Inc.

FERC


Direct Current Electricity

14-10b

Superposition Theorem

Example (FEIM):

Determine the current through the center leg of the circuit.

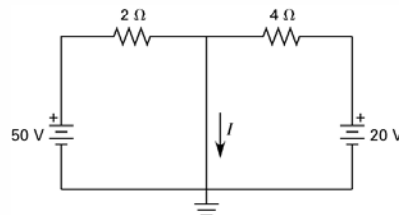Short the 20 V source. $I = 50 \frac{\text{V}}{2 \Omega} = 25 \text{ A}$ Short the 50 V source. $I = 20 \frac{\text{V}}{4 \Omega} = 5 \text{ A}$ $I_{\text{total}} = 25 \text{ A} + 5 \text{ A} = 30 \text{ A}$

Professional Publications, Inc.


FERC

Direct Current Electricity

14-11a

Norton Equivalent

Figure 44.4 Norton Equivalent Circuit

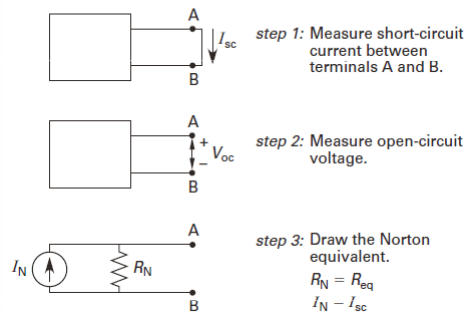

$$V_{\text{oc}} = V_A - V_B \quad 44.36$$

$$R_{\text{eq}} = \frac{V_{\text{oc}}}{I_{\text{sc}}} \quad 44.37$$

Professional Publications, Inc.

FERC


Direct Current Electricity

14-11b

Norton Equivalent

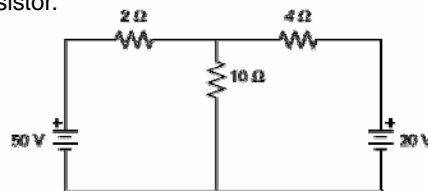Example (FEIM):

Find the Norton equivalent current and resistance of the circuit as seen by the $10\ \Omega$ resistor.



With the $10\ \Omega$ resistor open circuited, and the voltage sources shorted, the circuit is $4.0\ \Omega$ and $2.0\ \Omega$ in parallel.

$$R_N = (2\ \Omega) \left(\frac{4\ \Omega}{2\ \Omega + 4\ \Omega} \right) = 1.33\ \Omega$$

With the $10\ \Omega$ resistor shorted, the circuit looks just like the previous example.

$$I_N = 30\ \text{A}$$

Professional Publications, Inc.


FERC

Direct Current Electricity

14-12a

Thevenin Equivalent

Figure 44.3 Thevenin Equivalent Circuit

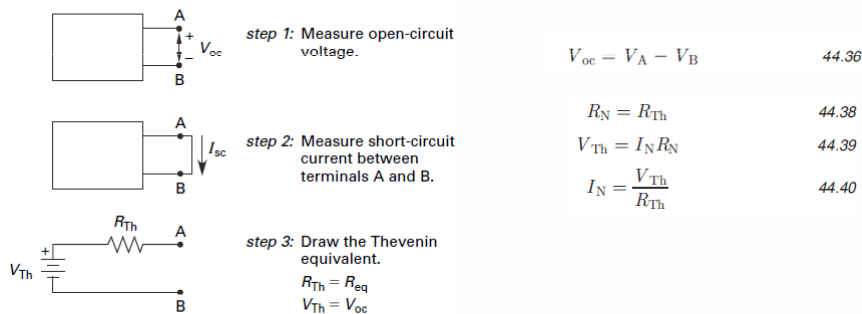

Professional Publications, Inc.

FERC


Direct Current Electricity

14-12b

Thevenin Equivalent

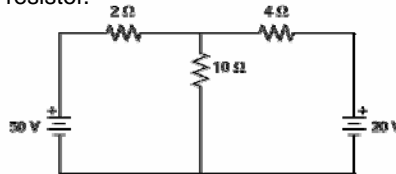Example (FEIM):

Find the Thevenin equivalent voltage and resistance of the circuit as seen by the $10\ \Omega$ resistor.



The Thevenin resistance is the same as the Norton resistance in the previous example, which is $1.3\ \Omega$. With the $10\ \Omega$ resistor open-circuited, apply the Kirchhoff voltage law around the loop and find $V_{TH} = 40\text{ V}$.


Professional Publications, Inc.

FERC

Direct Current Electricity

14-12c

Thevenin Equivalent

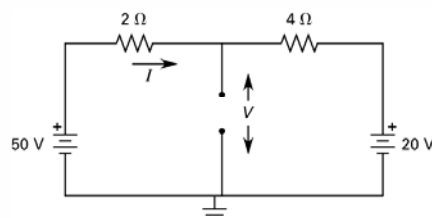

$$(50\text{ V} - 20\text{ V}) = I(2\ \Omega + 4\ \Omega)$$

$$I = 5\text{ A}$$

$$\begin{aligned} V &= 50\text{ V} - I(2\ \Omega) \\ &= 50\text{ V} - (5\text{ A})(2\ \Omega) \\ &= 40\text{ V} \end{aligned}$$

Professional Publications, Inc.

FERC

Direct Current Electricity

14-13a

Capacitors

$$q_C(t) = C v_C(t)$$

$$C = \frac{q_C(t)}{v_C(t)} \quad [\text{varying } v(t)] \quad 44.9$$

$$\begin{aligned} \text{energy} &= \frac{C v_C^2}{2} = \frac{q_C^2}{2C} \\ &= \frac{q_C v_C}{2} \end{aligned} \quad 44.13$$

Parallel Plate Capacitors

$$C = \frac{\epsilon A}{d} \quad 44.10$$

- Capacitance in Parallel:

$$C_P = C_1 + C_2 + \cdots + C_n \quad 44.19$$

- Capacitance in Series:

$$C_S = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2} + \cdots + \frac{1}{C_n}} \quad 44.18$$

Professional Publications, Inc.

FERC


Direct Current Electricity

14-13b

Capacitors

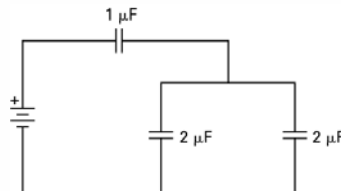Example 1 (FEIM):

What is the capacitance seen by the battery?



The two 2 μF capacitors in parallel are equivalent to 4 μF. The 1 μF capacitor in series with the equivalent 4 μF capacitance will add as resistors in parallel.

$$\begin{aligned} C &= \frac{C_1 C_2}{C_1 + C_2} \\ &= \frac{(1 \mu\text{F})(4 \mu\text{F})}{1 \mu\text{F} + 4 \mu\text{F}} \\ &= 4/5 \mu\text{F} \end{aligned}$$

Professional Publications, Inc.

FERC

Direct Current Electricity

14-13c

Capacitors

Example 2 (FEIM):

A $10\ \mu\text{F}$ capacitor has been connected to a potential source of $150\ \text{V}$.
 The energy stored in the capacitor in 10 time constants is most nearly

- (A) $1.0 \times 10^{-7}\ \text{J}$
- (B) $9.0 \times 10^{-3}\ \text{J}$
- (C) $1.1 \times 10^{-1}\ \text{J}$
- (D) $9.0 \times 10^1\ \text{J}$

$$\begin{aligned}\text{Energy} &= \frac{(10 \times 10^{-6}\ \text{F})(150\ \text{V})^2}{2} \\ &= 0.11\ \text{J} \quad (1.1 \times 10^{-1}\ \text{J})\end{aligned}$$

Therefore, the answer is (C).

Professional Publications, Inc.

FERC

Direct Current Electricity

14-14a

Inductors

$$L = \frac{N\phi}{i_L} \quad 44.14$$

$$v_L(t) = L \frac{di_L}{dt} \quad 44.15$$

$$i_L(t) = i_L(0) + \frac{1}{L} \int_0^{t_0} v_L(t) dt \quad 44.16$$

- Inductance in Series:

$$L_S = L_1 + L_2 + \cdots + L_n \quad 44.20$$

- Inductance in Parallel:

$$L_P = \frac{1}{\frac{1}{L_1} + \frac{1}{L_2} + \cdots + \frac{1}{L_n}} \quad 44.21$$

Professional Publications, Inc.

FERC


Direct Current Electricity

14-14b

Inductors

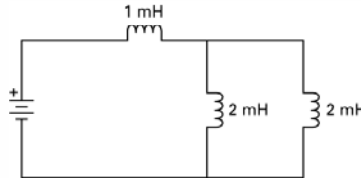Example (FEIM):

Find the inductance as seen from the battery.



The two 2 mH inductors in parallel will add as resistors in parallel.

$$L = \frac{L_1 L_2}{L_1 + L_2} = \frac{(2 \text{ mH})(2 \text{ mH})}{2 \text{ mH} + 2 \text{ mH}} = 1 \text{ mH}$$

The 1 mH inductor in series with the equivalent 1 mH inductance will combine for 2 mH total inductance.

Professional Publications, Inc.



FERC

Direct Current Electricity

14-15a

RC Transients

Figure 44.5 RC Transient Circuit

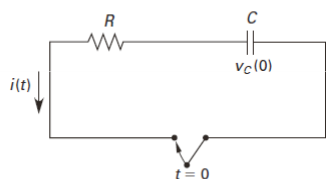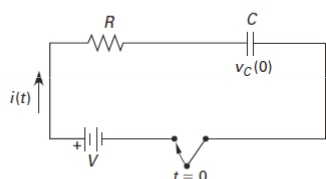(a) series-RC, discharging
(energy source(s) disconnected)(b) series-RC, charging
(energy source(s) connected)

$$v_C(t) = v_C(0)e^{-t/RC} + V(1 - e^{-t/RC}) \quad 44.45$$

$$i(t) = \left(\frac{V - v_C(0)}{R} \right) e^{-t/RC} \quad 44.46$$

$$\begin{aligned} v_R(t) &= i(t)R \\ &= (V - v_C(0))e^{-t/RC} \end{aligned} \quad 44.47$$

Professional Publications, Inc.

FERC

Direct Current Electricity


14-15b

RC Transients

Example (FEIM):

At $t = 0$, the capacitor is discharged, and the switch is moved from A to B. At $t = 6$ s, the switch is moved to C.

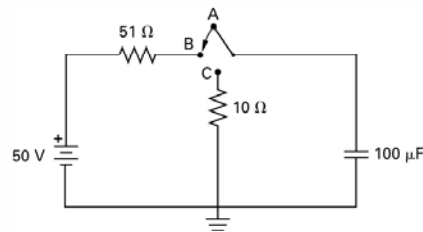- (a) What is the capacitor voltage at $t = 6$ s?
- (b) What is the current at $t = 10$ s?
- (c) When (after 6 s) is the voltage across the capacitor equal to 10 V?



Professional Publications, Inc.

FERC

Direct Current Electricity

14-15c

RC Transients

- (a) From time = 0 to 6 s,

$$V_c(0) = 0$$

$$V = 50 \text{ V}$$

$$RC = (51 \times 10^3 \Omega)(100 \times 10^{-6} \text{ F}) = 5.1 \text{ s}$$

$$v_c(6 \text{ s}) = 0e^{-\frac{6 \text{ s}}{5.1 \text{ s}}} + 50 \text{ V} \left(1 - e^{-\frac{6 \text{ s}}{5.1 \text{ s}}} \right) = 34.58 \text{ V}$$

So 34.58 V is the peak voltage the capacitor reaches before it starts to discharge.

Professional Publications, Inc.

FERC

Direct Current Electricity

14-15d

RC Transients

(b) From time = 6 s on,

$$V_c(6\text{ s}) = 34.58\text{ V}$$

$$V = 0\text{ V}$$

$$RC = (10 \times 10^3 \Omega)(100 \times 10^{-6} \text{ F}) = 1\text{ s}$$

$$i(10\text{ s}) = \left(\frac{0 - 34.58\text{ V}}{10 \times 10^3 \Omega} \right) e^{\frac{-10\text{ s} - 6\text{ s}}{1}} = -6.3 \times 10^{-5}\text{ A}$$

$$(c) v_c(t) = 34.58\text{ V} e^{\frac{t-6\text{ s}}{-1\text{ s}}} + 0 \left(1 - e^{\frac{t-6\text{ s}}{-1\text{ s}}} \right) = 10\text{ V}$$

Take the natural logarithm of both sides of the equation

$$\ln 34.58\text{ V} e^{-(t-6\text{ s})} = \ln 10$$

$$\ln e^{-(t-6\text{ s})} + \ln 34.58\text{ V} = \ln 10$$

$$-(t-6\text{ s}) = \ln 10 - \ln 34.58\text{ V}$$

$$t - 6\text{ s} = 1.24\text{ s}$$

$$t = 7.24\text{ s}$$

Professional Publications, Inc.



FERC

Direct Current Electricity

14-16a

RL Transients

Figure 44.6 RL Transient Circuit

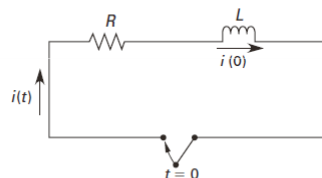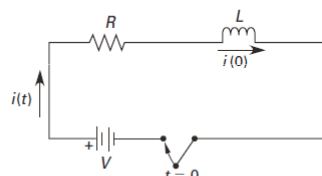(a) series-RL, discharging
(energy source(s) disconnected)(b) series-RL, charging
(energy source(s) connected)

$$v_R(t) = i(t)R$$

$$= i(0)R e^{-Rt/L} + V(1 - e^{-Rt/L}) \quad 44.48$$

$$i(t) = i(0)e^{-Rt/L} + \frac{V}{R}(1 - e^{-Rt/L}) \quad 44.49$$

$$v_L(t) = L \frac{di}{dt}$$

$$= -i(0)R e^{-Rt/L} + V e^{-Rt/L} \quad 44.50$$

Professional Publications, Inc.

FERC


Direct Current Electricity

14-16b

RL Transients

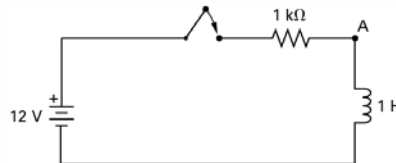Example (FEIM):

Find the voltage at point A at the instant the switch is closed. The switch has been open for a long time, and there is no initial current in the inductor.



- (A) 0 V
- (B) 1 V
- (C) 3 V
- (D) 12 V

$$i(0) = 0$$

$$V = 12 \text{ V, so at } t = 0$$

$$v_L(0^+) = 0Re^0 + (12 \text{ V})e^0 = 12 \text{ V}$$

Therefore, the answer is (D).

Professional Publications, Inc.

FERC

Direct Current Electricity

14-17

Transducers

A transducer is any device used to convert a physical phenomenon into an electrical signal (e.g., microphone, thermocouple, and voltmeter).

Characteristics of measurement design:

- Sensitivity
- Linearity
- Accuracy
- Precision
- Stability

Professional Publications, Inc.

FERC

Direct Current Electricity**14-18a****Resistance Temperature Detectors (RTDs)**

Make use of changes in their resistance to determine the changes in temperature.

$$R_T = R_0(1 + \alpha(T - T_0)) \quad 49.3$$

Example (FEIM):

A resistance temperature detector (RTD) that is not perfectly linear is used for a temperature measurement. The temperature coefficient is $3.900 \times 10^{-3} \text{ } ^\circ\text{C}^{-1}$, the reference temperature is 0°C , and the reference resistance is $500.0 \text{ } \Omega$. The resistance measured when the actual temperature is 400°C is $1247 \text{ } \Omega$. Determine the error in the temperature measurement.

Professional Publications, Inc.

FERC

Direct Current Electricity**14-18b****Resistance Temperature Detectors (RTDs)**

If the RTD was perfectly linear the resistance would be given by

$$R_T = R_0(1 + \alpha(T - T_0))$$

However, the temperature that the RTD indicates is not the actual temperature of 400°C , so rearranging the RTD equation to solve for the temperature that the RTD indicates yields

$$\begin{aligned} T &= \frac{R_T - R_0 + \alpha R_0 T_0}{\alpha R_0} \\ &= \frac{1247 \text{ } \Omega - 500.0 \text{ } \Omega + (3.900 \times 10^{-3} \text{ } ^\circ\text{C}^{-1})(500^\circ\text{C})(0^\circ\text{C})}{(3.900 \times 10^{-3} \text{ } ^\circ\text{C}^{-1})(500^\circ\text{C})} \\ &= 383.1^\circ\text{C} \end{aligned}$$

The error in the measurement is:
Error = $383.1^\circ\text{C} - 400^\circ\text{C} = -16.9^\circ\text{C}$

Professional Publications, Inc.

FERC

Direct Current Electricity

14-19a

Strain Gages

Metal or semiconductor foils that change resistance linearly with the strain.

$$GF = \frac{\frac{\Delta R}{R}}{\frac{\Delta L}{L}} = \frac{\frac{\Delta R}{R}}{\epsilon} \quad 49.6$$

Example (FEIM):

A strain gage is measured to determine the gage factor. A strain gage with an initial resistance of $200.00 \, \Omega$ and final resistance of $199.79 \, \Omega$ when subjected to a strain that causes the gage to compress to 0.9994 cm. The initial length of the gage was 1.0000 cm. What is the gage factor?

- (A) 0.15
- (B) 0.42
- (C) 1.8
- (D) 4.0

Professional Publications, Inc.

FERC

Direct Current Electricity

14-19b

Strain Gages

$$GF = \frac{\frac{\Delta R}{R}}{\frac{\Delta L}{L}}$$

$$= \frac{\frac{199.79 \, \Omega - 200.00 \, \Omega}{200.00 \, \Omega}}{\frac{0.9994 \, \text{cm} - 1.0000 \, \text{cm}}{1.0000 \, \text{cm}}}$$

$$= 1.75$$

Therefore, the answer is (C).

Professional Publications, Inc.

FERC

Direct Current Electricity

14-20a


Wheatstone Bridges

Balanced:

$$R_1 R_4 = R_2 R_3 \quad [\text{balanced}] \quad 49.11$$

Quarter-bridge:

Figure 49.3 Wheatstone Quarter Bridge

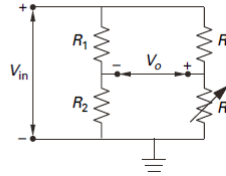

$$R_1 = R_2 = R_3 = R \quad 49.12$$

$$R_4 = R + \Delta R \quad 49.13$$

$$\Delta R \ll R \quad 49.14$$

$$V_o \approx \left(\frac{\Delta R}{4R} \right) V_{in} \quad 49.15$$

Professional Publications, Inc.

FERC

Direct Current Electricity

14-20b

Wheatstone Bridges

Example (FEIM):

There are three high-precision resistors known to be 10.00 kΩ in a quarter bridge circuit. R_1 is a sensor with a small resistance difference from 10 kΩ. Find the resistance if $V_{in} = 5.00$ V and $V_o = 0.03$ V.

$$\begin{aligned} \Delta R &= \frac{4RV_o}{V_{in}} \\ &= \frac{(4)(10.00 \text{ k}\Omega)(0.03 \text{ V})}{5.00 \text{ V}} \\ &= 0.24 \text{ k}\Omega \end{aligned}$$

$$R_1 = 10.00 \text{ k}\Omega + 0.24 \text{ k}\Omega = 10.24 \text{ k}\Omega$$

For the strain gage quarter-bridge circuit, ΔR can be substituted.

$$V_o = \frac{1}{4}(\text{GF})\epsilon V_{in}$$

Professional Publications, Inc.

FERC

Direct Current Electricity

14-21a

Sampling

Sampling Rate or Frequency:

$$f_s = \frac{1}{\Delta t}$$

49.16

Shannon's Sampling Theorem

Determines the sampling rate to reproduce accurately in the discrete time system.

Nyquist Rate:

$$f_N = 2f_i$$

49.17

(where f_i is the frequency of interest)

Reproducible Sampling:

$$f_s > f_n \quad [\text{reproducible sampling}]$$

Professional Publications, Inc.

FERC

Direct Current Electricity

14-21b

Sampling

Example (FEIM):

An analog signal is to be sampled at $0.03 \mu\text{s}$ intervals. What is most nearly the highest frequency that can be accurately reproduced?

- (A) $4.0 \times 10^6 \text{ Hz}$
- (B) $12 \times 10^6 \text{ Hz}$
- (C) $16 \times 10^6 \text{ Hz}$
- (D) $18 \times 10^6 \text{ Hz}$

The sampling frequency is

$$\begin{aligned} f_s &= \frac{1}{\Delta t} \\ &= \frac{1}{0.03 \times 10^{-6}} \\ &= 33 \times 10^6 \text{ Hz} \end{aligned}$$

Professional Publications, Inc.

FERC

Direct Current Electricity

14-21c

Sampling

The sampling frequency must be greater than the Nyquist rate for accurate reproduction.

$$f_s > 2f_N$$

The greatest frequency that can be reproduced at this sampling rate is

$$f_N < \frac{f_s}{2} = \frac{33 \times 10^6 \text{ Hz}}{2} = 16.7 \times 10^6 \text{ Hz} \quad (16 \times 10^6 \text{ Hz})$$

Therefore, the answer is (C).

Professional Publications, Inc.

FERC

Direct Current Electricity

14-22a

Analog-to-Digital Conversion

Voltage Resolution

The range from a high voltage, V_H , and a low voltage, V_L , is divided up into the 2^n ranges.

$$\epsilon_V = \frac{V_H - V_L}{2^n} \quad 49.19$$

For example, if all the bits are "1" then the analog value is somewhere between V_H and $V_H - \epsilon_V$. To calculate the analog value from the digital value use

$$V = \epsilon_V N + V_L \quad 49.20$$

Professional Publications, Inc.

FERC

Direct Current Electricity

14-22b

Analog-to-Digital Conversion

Example (FEIM):

A 16 bit analog-to-digital conversion has a resolution of 1.52588×10^{-4} V and the lowest voltage measured has half the magnitude of the highest voltage. Both the high and low voltages are positive. Determine the highest voltage.

$$\begin{aligned} V_H - V_L &= 2^n \varepsilon_v \\ &= (2)^{16} (1.52588 \times 10^{-4} \text{ V}) \\ &= 10.0 \text{ V} \end{aligned}$$

The problem statement also says that

$$|V_H| = |2V_L|$$

Since V_H and V_L are positive, this equation becomes

$$V_H = 2V_L$$

Substituting into the first equation

$$2V_L - V_L = 10 \text{ V}$$

$$V_L = 10 \text{ V}$$

$$V_H = 20 \text{ V}$$

Professional Publications, Inc.

FERC

Direct Current Electricity

14-23a

Measurement Uncertainty

Kline-McClintock Equation:

A method for estimating the uncertainty in a function that depends on more than one measurement.

$$w_R = \sqrt{\left(w_1 \frac{\partial f}{\partial x_1}\right)^2 + \left(w_2 \frac{\partial f}{\partial x_2}\right)^2 + \cdots + \left(w_n \frac{\partial f}{\partial x_n}\right)^2} \quad 49.21$$

Professional Publications, Inc.

FERC

Direct Current Electricity

14-23b

Measurement Uncertainty

Example (FEIM):

A function is given by $R = 5x_1 - 3x_2^2$.

Find the measurement uncertainty at (1, 2) if the uncertainty in the variables is ± 0.01 and ± 0.03 respectively.

$$\frac{\partial R}{\partial x_1} = 5 \quad \frac{\partial R}{\partial x_2} = -6x_2$$

At the point (1, 2) the partial derivatives are

$$\left. \frac{\partial R}{\partial x_1} \right|_{(1,2)} = 5 \quad \left. \frac{\partial R}{\partial x_2} \right|_{(1,2)} = (-6)(2) = -12$$

$$\begin{aligned} w_R &= \sqrt{\left(w_1 \left. \frac{\partial R}{\partial x_1} \right|_{(1,2)} \right)^2 + \left(w_2 \left. \frac{\partial R}{\partial x_2} \right|_{(1,2)} \right)^2} \\ &= \sqrt{((0.01)(5))^2 + ((0.03)(-12))^2} \\ &= 0.36 \end{aligned}$$

Professional Publications, Inc.

FERC

Direct Current Electricity

14-23c

Measurement Uncertainty

If the function R is the sum of the measurements,

$R = x_1 + x_2 + x_3 + \dots + x_n$, then the Kline-McClintock method reduces to

$$w_R = \sqrt{w_1^2 + w_2^2 + \dots + w_n^2}$$

This is called the *root sum square* (RSS) value.

If the function R is the sum of the measurements times constants,

$R = a_1x_1 + a_2x_2 + a_3x_3 + \dots + a_nx_n$, then the Kline-McClintock method reduces to

$$w_R = \sqrt{a_1^2 w_1^2 + a_2^2 w_2^2 + \dots + a_n^2 w_n^2}$$

This is called a *weighted* RSS value.

Professional Publications, Inc.

FERC